

Chapter 26

- Direct-Current (DC) Circuits

Michael Wong – PHY 1122 Spring 2023

Learning goals

- Resistors in **series** and **parallel**
- **Kirchhoff's rules** for circuit analysis
- Measuring current, voltage, resistance in a circuit
- Analyzing **RC circuits**.

Electric circuit analysis

- We will learn general methods for analyzing complex networks of circuit elements
 - Batteries, resistors, capacitors, etc...
 - Kirchhoff's rules (based on conservation of charge, energy)
- Resistors in series and parallel – similar (but opposite) rules compared to capacitors.
- We analyze circuits with DC (direct current)

DC vs AC

- **Direct Current** (DC) in a circuit has constant direction.
 - We analyze circuits where things are in *steady state* (constant magnitude and direction of current).
- A battery produces DC voltage, household wall sockets provide alternating current (AC) voltage.
 - Adapters convert AC to DC to power your phone, laptop, *sewing machine*, etc...

Resistors in series

- Resistors in **series** are connected one after the other, current is the same:


$$I = I_1 = I_2$$

- The voltage adds up:

$$V_{ab} = V_{ax} + V_{xy} + V_{yb}$$


$$V_{ab} = IR_1 + IR_2 + IR_3 = I(R_1 + R_2 + R_3) = IR_{eq}$$

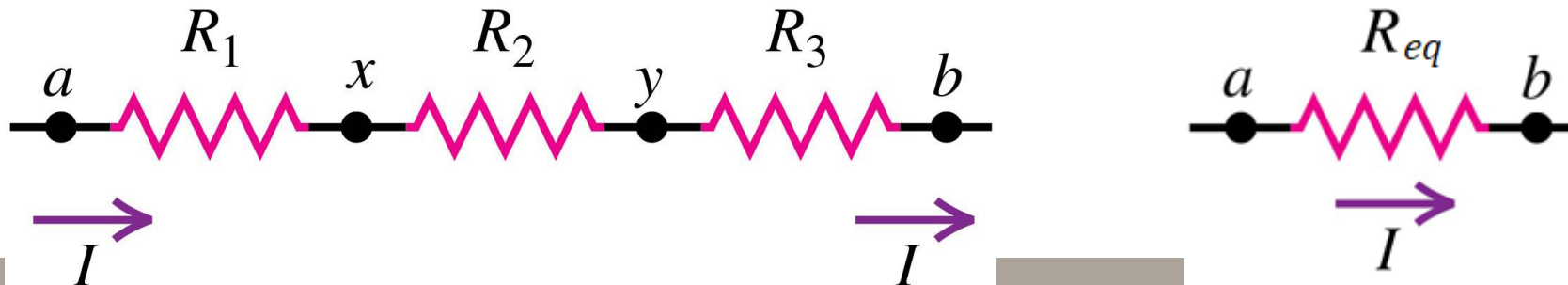- We see that the equivalent resistance is: $R_{eq} = R_1 + R_2 + \dots$



Resistors in series (notes)

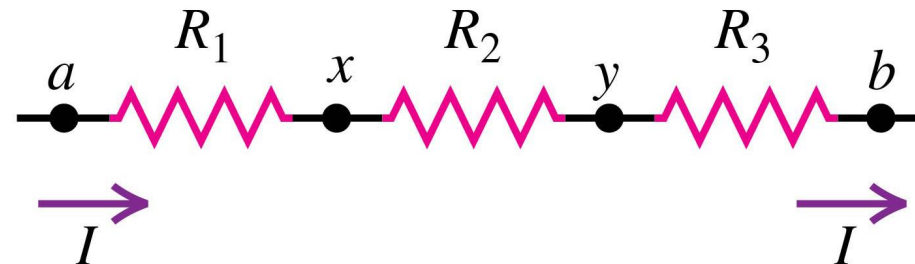- If one device in a series circuit fails, all devices will stop working (cheap old Christmas lights).
- A local change in one part may result in a global change throughout.
 - Change R_1 and the voltage in all other resistors and the terminal voltage of battery will change.
- In series circuit, only one path for current to take.
 - Hence why $I = I_1 = I_2 = \dots$



Resistors in parallel

- For resistors in **parallel**, potential difference between each is the same:

$$V_{ab} = V_1 = V_2 = V_3$$

- The current is summed:



$$I = I_1 + I_2 + I_3$$

$$I = \left(\frac{V_1}{R_1} \right) + \left(\frac{V_2}{R_2} \right) + \left(\frac{V_3}{R_3} \right)$$

$$I = V_{ab} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = V_{ab} \frac{1}{R_{eq}}$$


- The equivalent resistance is thus:
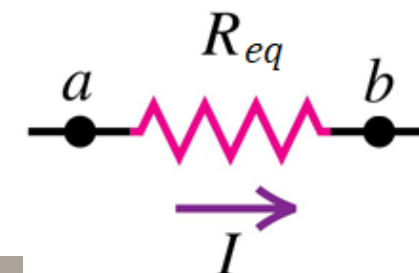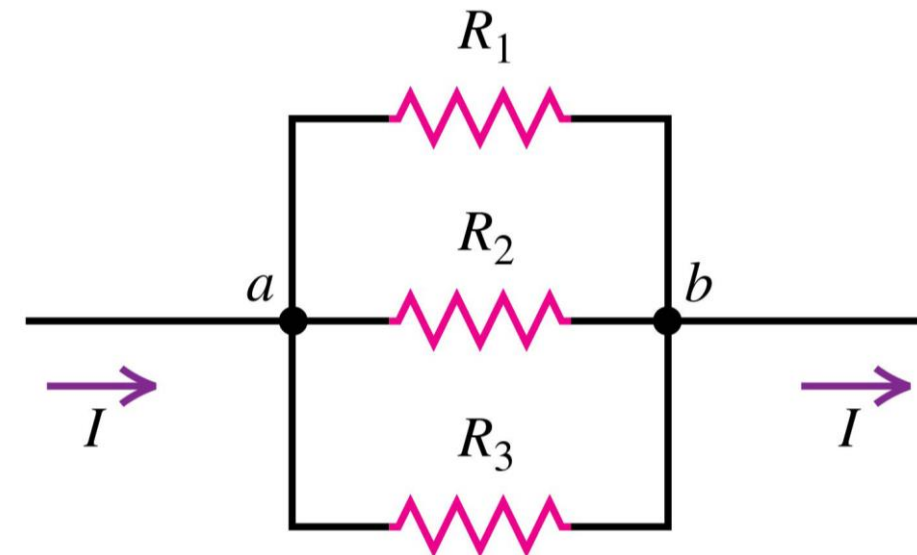
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$



Resistors in parallel (notes)

- Each device operates independently of the others
→ if one switched off, others remain on
- The current takes all paths in a circuit.
 - Lower R has higher I (path of least resistance)
 - I.e. Short circuit as shown in the bottom pic.
- Household circuits typically wired so that electrical devices are connected in parallel.

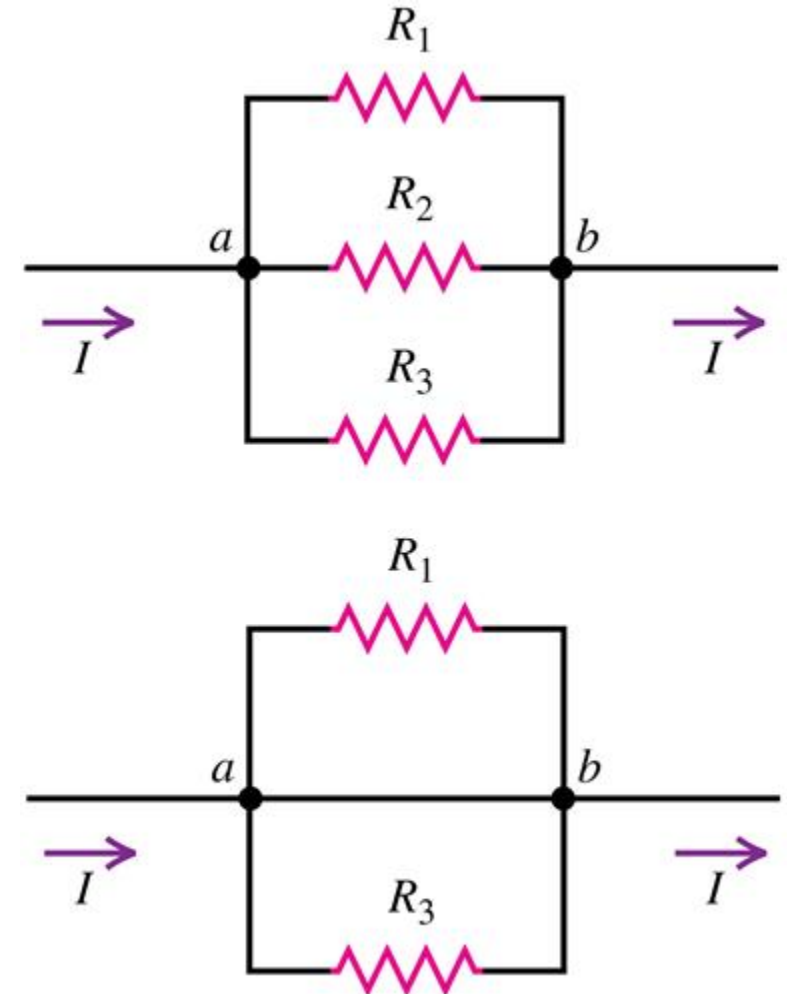


Ex. 26.2 – Series vs parallel

- Two light bulbs each with $R = 2\ \Omega$ are connected to source with $\mathcal{E} = 8\text{ V}$ and negligible internal resistance. Find the current I and voltage V through each bulb, and power P delivered for:


- (a) series connection
- (b) parallel connection

(c) Suppose one bulb burns out, what happens in each case (series vs parallel)?

(a) Light bulbs in series

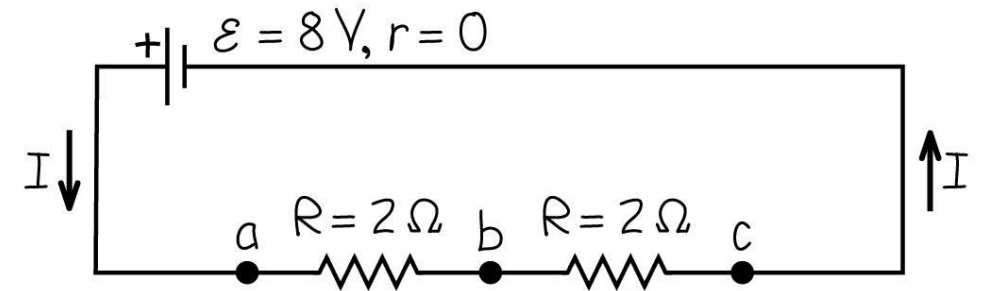


(b) Light bulbs in parallel

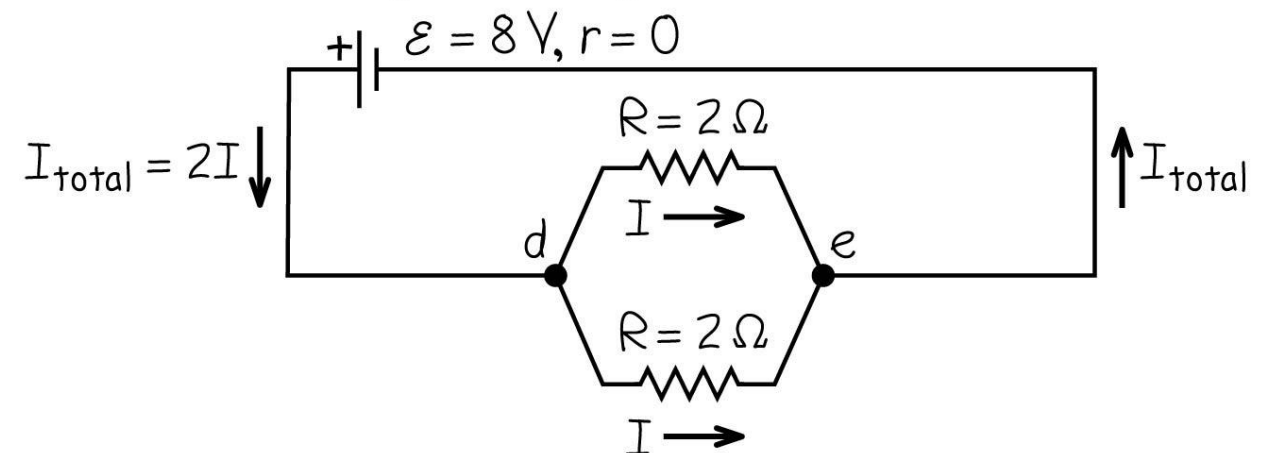


Ex. 26.2 – Series vs parallel (cont.)

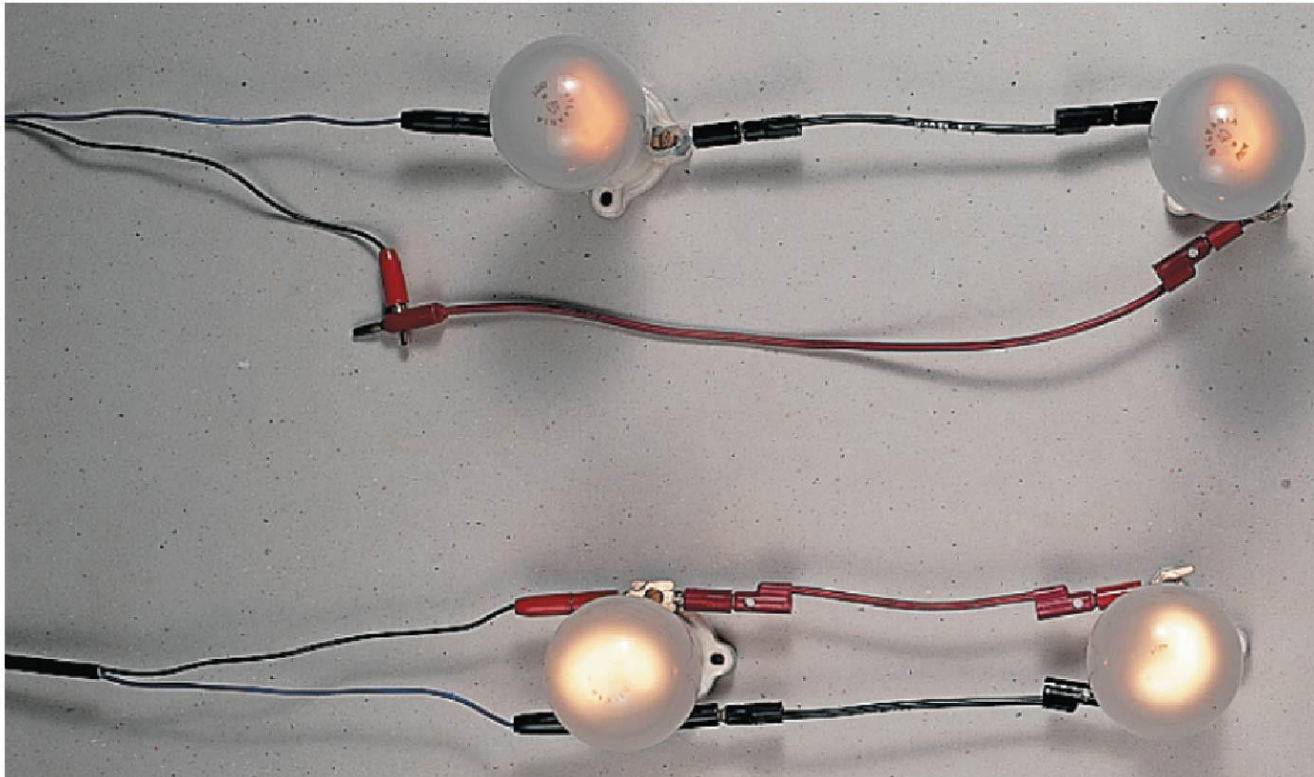- When connected to same source, two bulbs in series (top) draw less power and are dimmer compared to parallel connection (below).




Series and parallel combinations

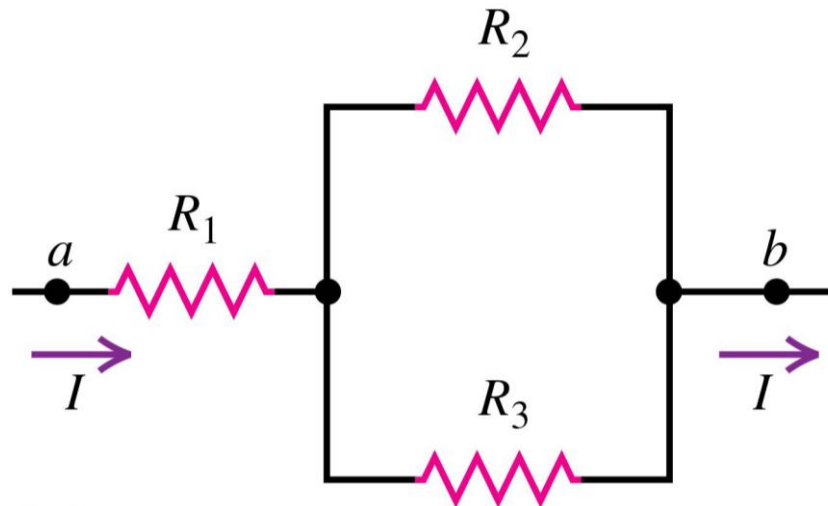- We can reduce these simple combinations:




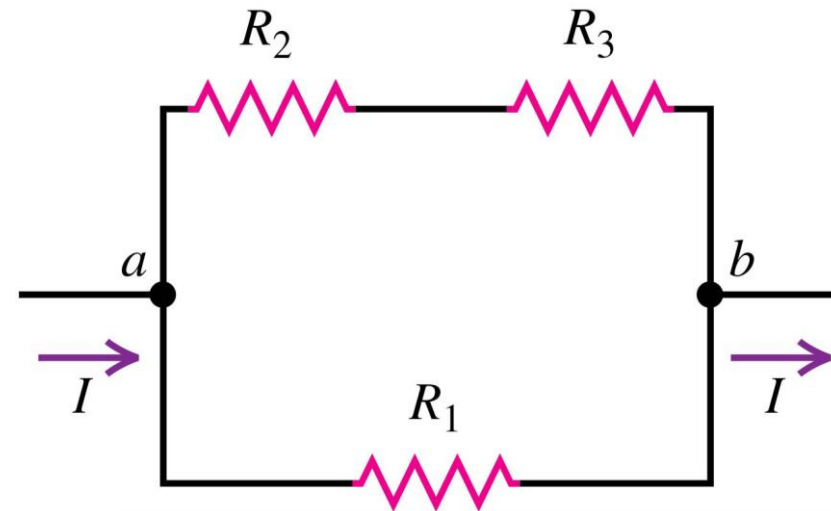
$$R_{eq1} = R_1 + \frac{1}{\frac{1}{R_2} + \frac{1}{R_3}}$$



$$R_{eq2} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2 + R_3}}$$


Tricky circuit drawings...

- Are the two circuits below equivalent?

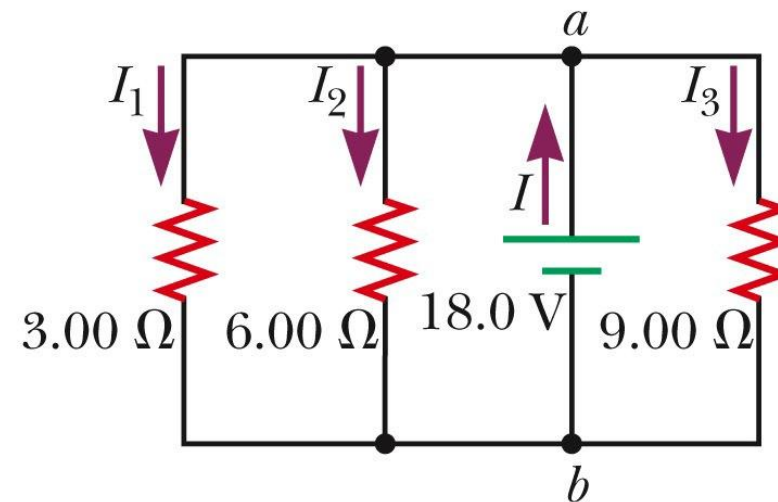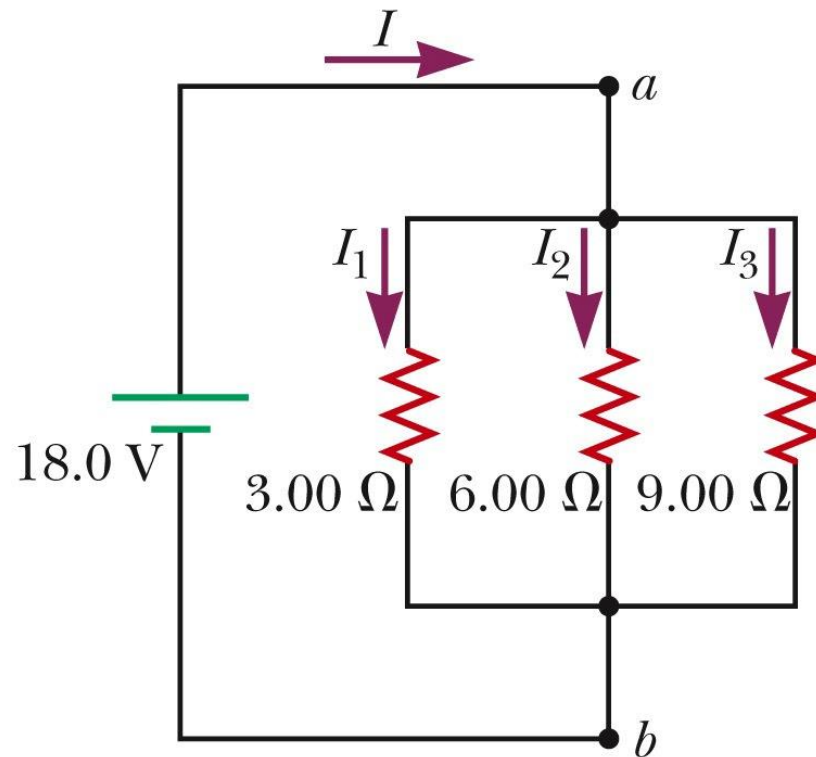

Kirchhoff's rules for circuit analysis


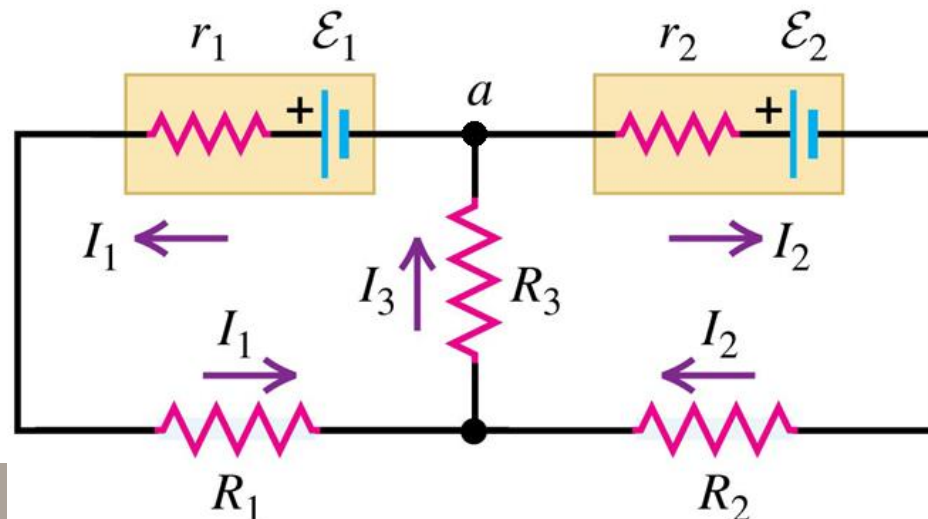
- Sometimes we have a complicated circuit which we can't reduce down to a single R_{eq} .
 - Ie. Circuit with multiple voltage sources.
- We use two rules, called **Kirchhoff's Rules**, to analyze.
 - Based on conservation of charge (**Junction rule**) and conservation of energy (**Loop rule**).



Kirchhoff's rules – Junction


- A **junction** is a point where three or more wires (conductors) meet.
- The sum of the currents at any junction equals zero.
 - Current directed into the junction is positive (+I)
 - Current leaving the junction is negative (-I)

$$\sum_{\text{junction}} I = 0$$

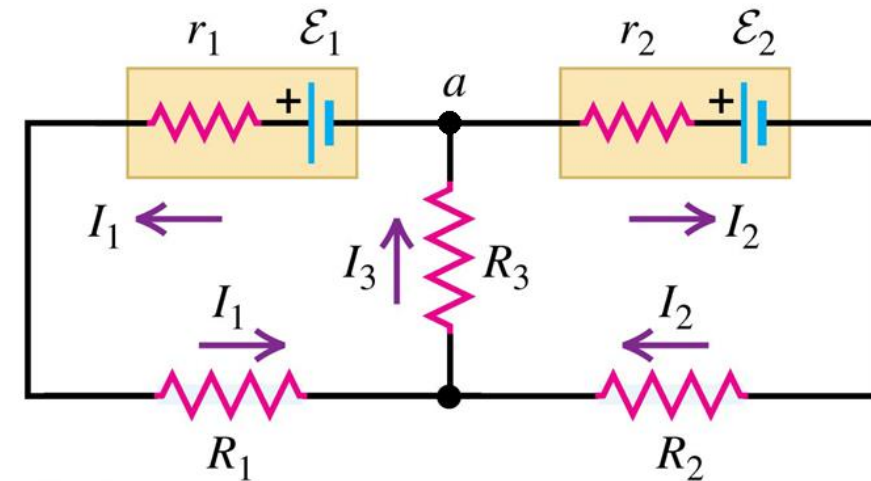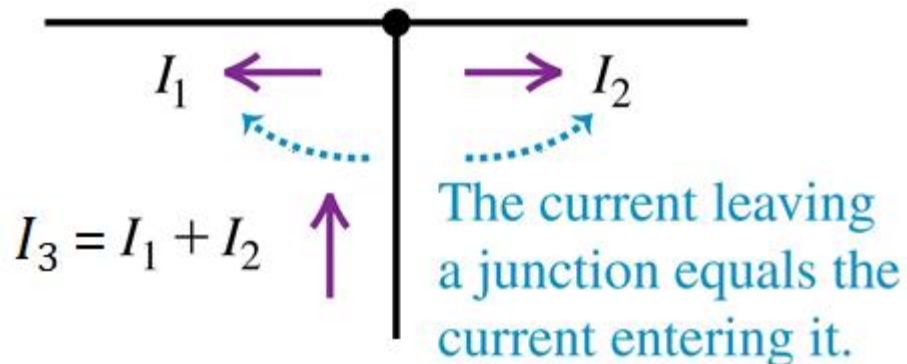

At a , $0 = I_3 - I_1 - I_2$

$$I_3 = I_1 + I_2$$

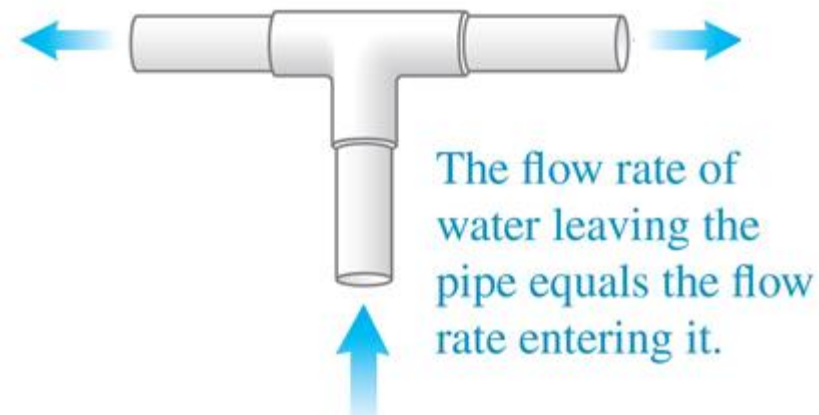


Kirchhoff's rules – Loop

- A **loop** is any closed conducting path.
- The sum of the potential differences across all elements around any closed loop must be zero,

$$\sum_{\text{closed loop}} \Delta V = 0$$

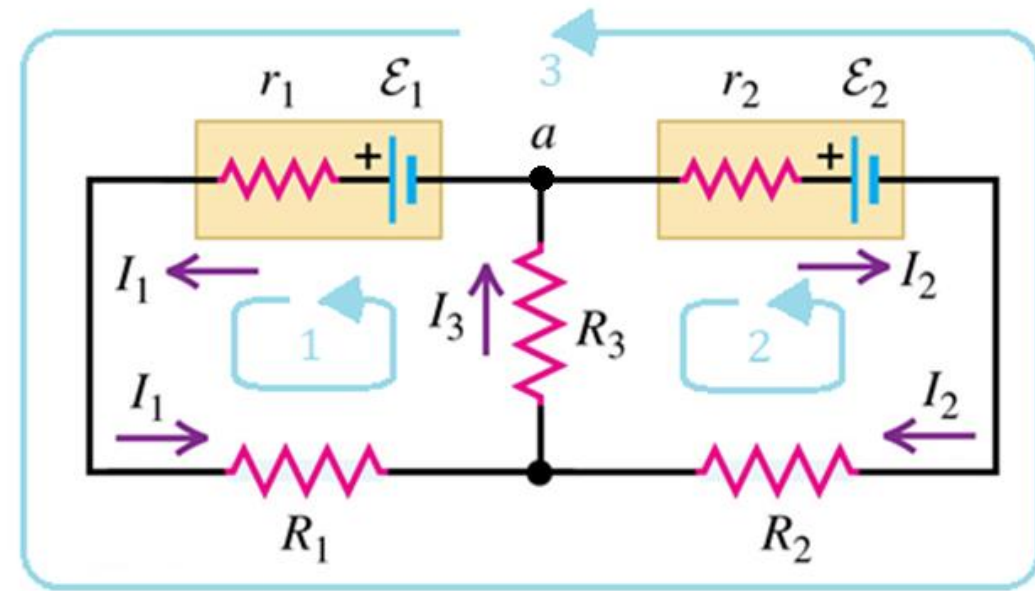
- The sign convention for the loop rule is very important!
(next slide)




Loop rule – sign convention

- For **emf** sources,
 “travel” from $-$ to $+$ $\rightarrow +\mathcal{E}$
 “travel” from $+$ to $-$ $\rightarrow -\mathcal{E}$
- For **resistors**,
 “travel” against $I \rightarrow V = +IR$
 “travel” with $I \rightarrow V = -IR$
- “Travel” is the direction we imagine going around the loop with.
 - Not necessarily same direction as I .

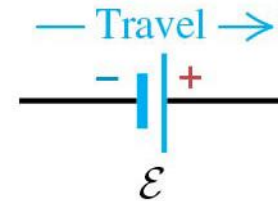
$+\mathcal{E}$: Travel direction
from $-$ to $+$:



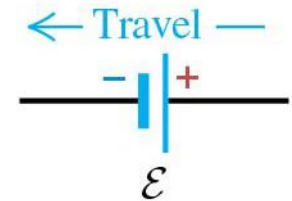
$-\mathcal{E}$: Travel direction
from $+$ to $-$:



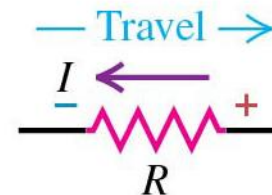$+IR$: Travel *opposite*
to current direction:



$-IR$: Travel *in*
current direction:

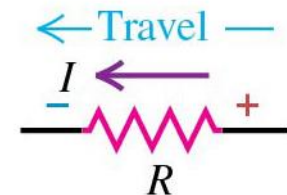

Loop rule equations

*Junction rule equation $I_3 = I_1 + I_2$

- For the **left** small loop 1, starting from the top right corner and traveling counterclockwise:

$$+\varepsilon_1 - I_1(r_1 + R_1) - I_3R_3 = 0$$


- For the **right** small loop 2, starting from the top right corner and traveling counterclockwise:

$$+\varepsilon_2 + I_3R_3 + I_2(r_2 + R_2) = 0$$

- For the **full** loop 3 starting from top right corner and traveling counterclockwise.


$$+\varepsilon_2 + \varepsilon_1 - I_1(r_1 + R_1) + I_2(r_2 + R_2) = 0$$

- It's possible the directions for the current are not correct! When solving you will get a *negative* value of current if you chose wrong.

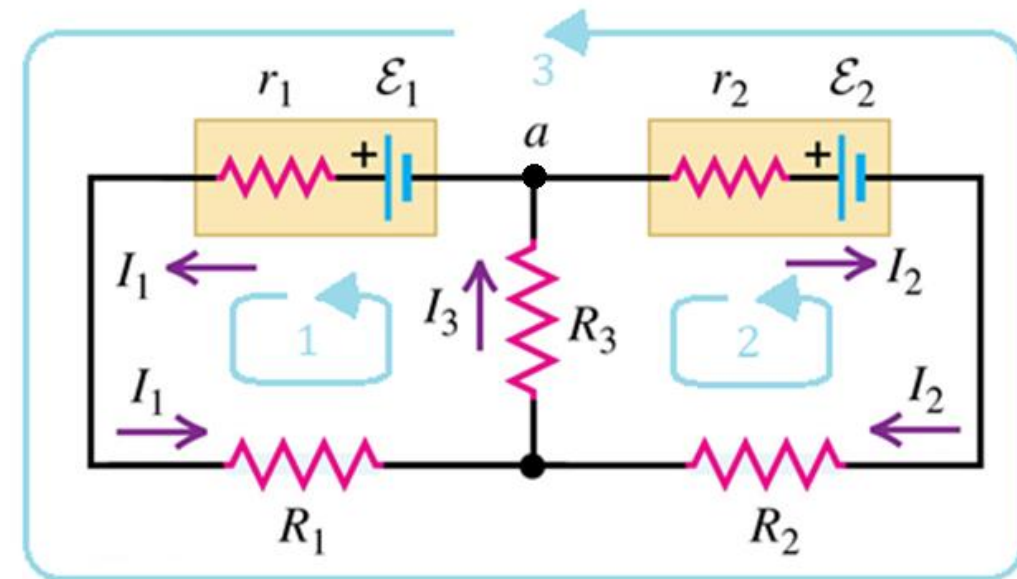





Ex. 26.6 – Complex network

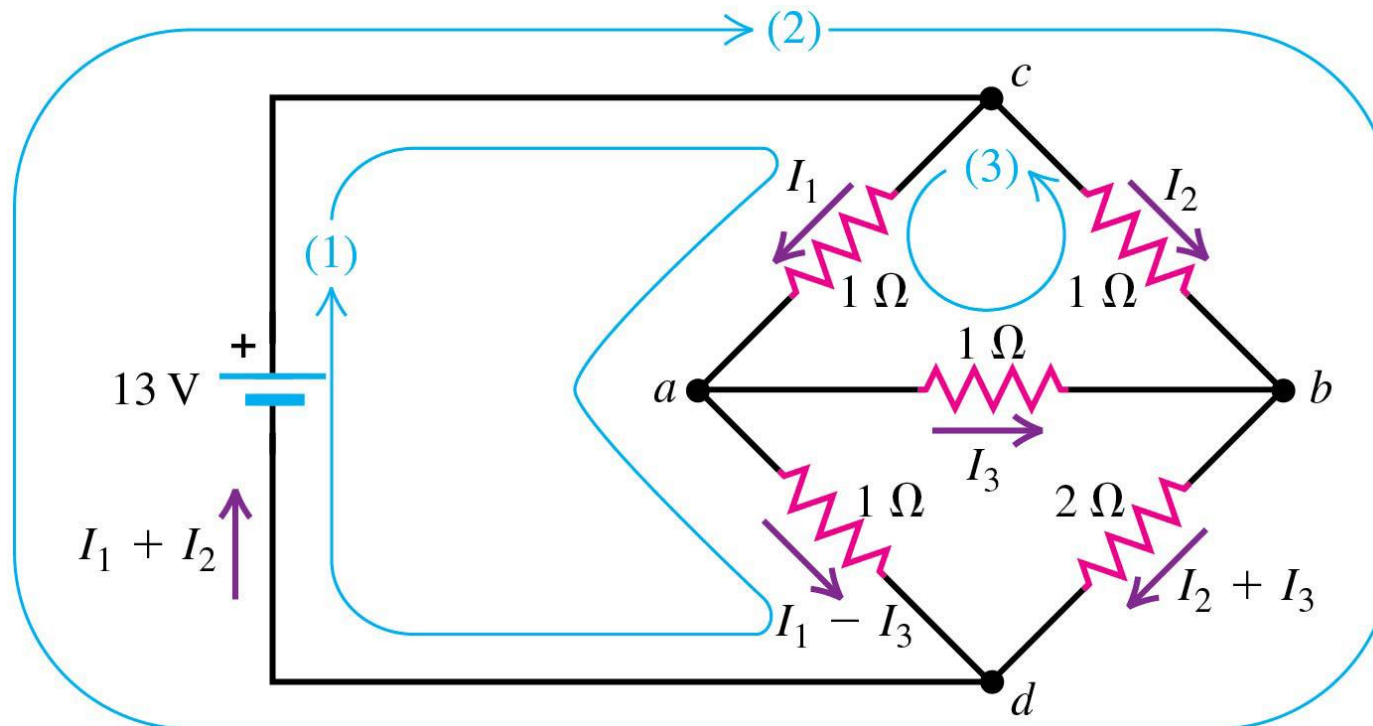- The figure shows a “bridge” circuit. Use Kirchhoff’s rules to find the current in each resistor and the equivalent resistance of the network of five resistors.






Electrical measuring instruments

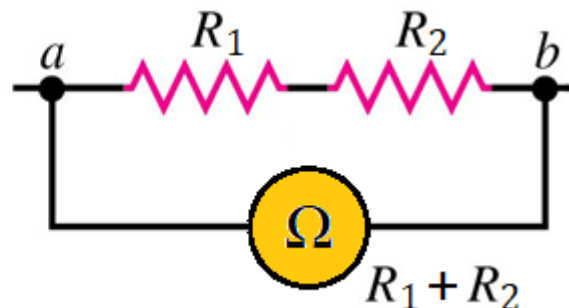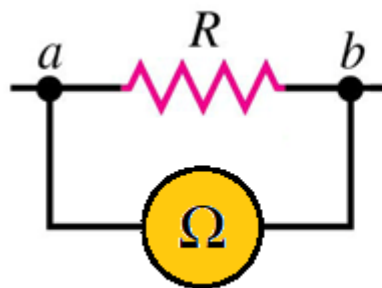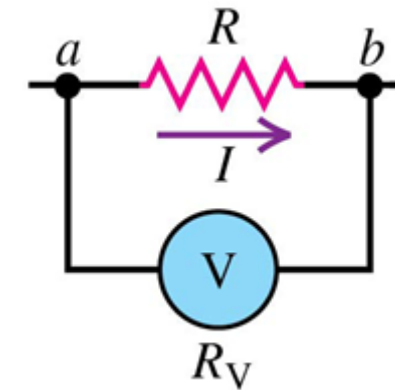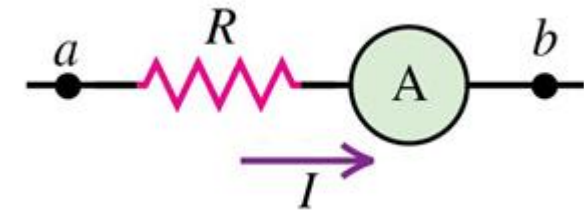- An **ammeter** measures the current passing through it. Must be connected in series with the circuit elements.
- A **voltmeter** measures the potential difference (voltage) between two points. Must be connected in parallel with circuit elements.
- An **ohmmeter** measures the resistance of a resistor or combination of resistors. Must be connected in parallel.



R-C circuits

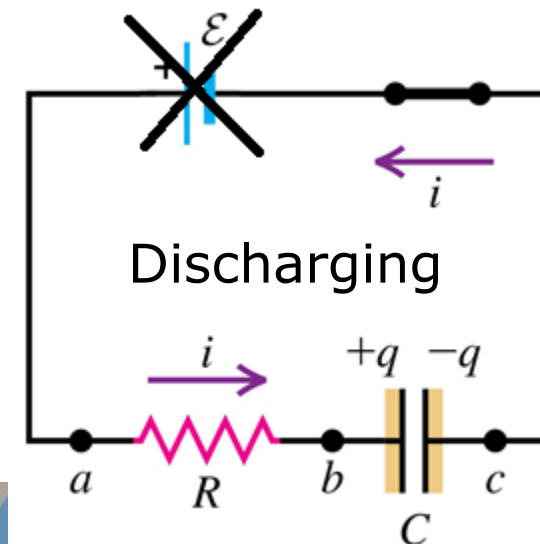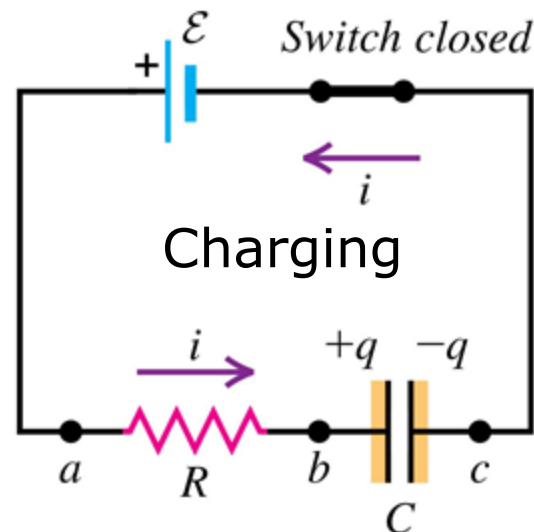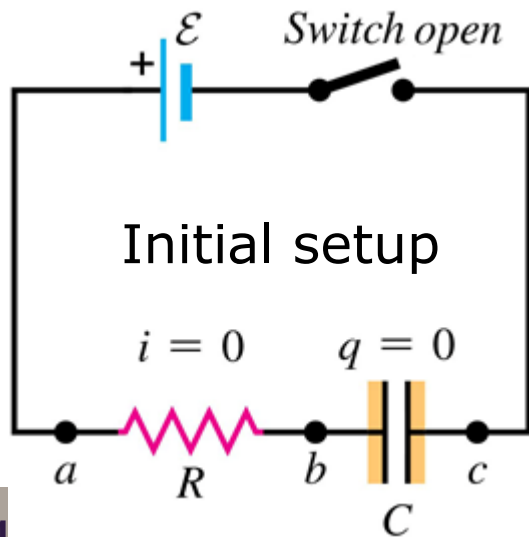- In a DC circuit with a capacitor, the current *may vary with time*.
 - Magnitude will change (not direction).
- An **RC circuit** combines a capacitor and resistor in series.
- Two situations to consider: **charge** and **discharge**.



R-C circuits – Charging

- Circuit is complete (at time $t = 0$), **charging** begins.
 - Constant emf, zero r , wires have no R .


- At $t = 0$, $Q_i = 0$ and $I_0 = \varepsilon/R$.

- As t increases, Q increases, i decreases.

- Eventually, charge is max and current is 0.

$$Q_f = C\varepsilon, i = 0$$

- How do q and i vary with time?

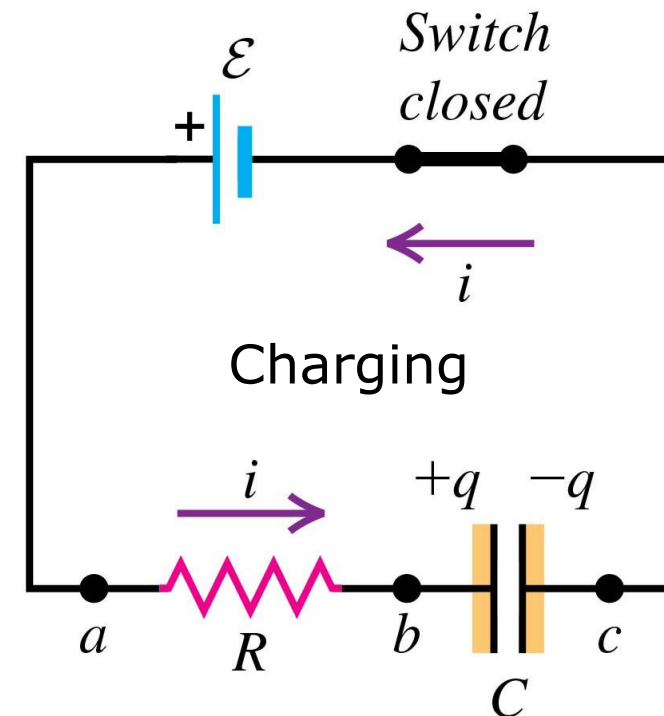


R-C circuits – Charging

- Analysis: start with loop rule, $\varepsilon - iR - \frac{q}{C} = 0$, then solve for i and set $i = dq/dt$. Separate dq and dt then integrate both sides.

$$\boxed{q_c} = C\varepsilon(1 - e^{-t/RC}) = \boxed{Q_f(1 - e^{-t/RC})}$$


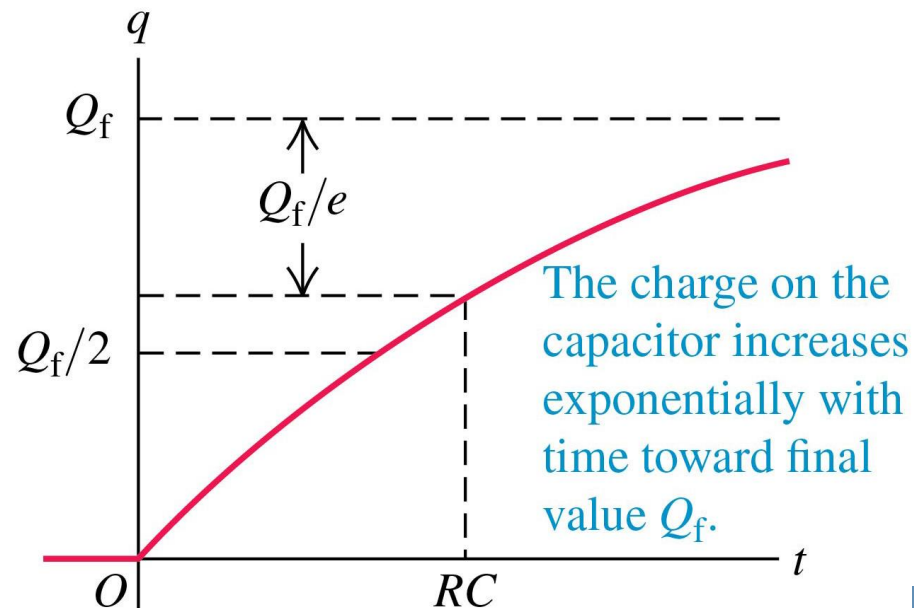
- We see that the charge increases exponentially with $(1 - e^{-x})$ relationship.
- We call $t = \boxed{\tau = RC}$ the time constant of the circuit.



R-C circuits – Charging

- The charge increases exponentially and the current will decrease exponentially:
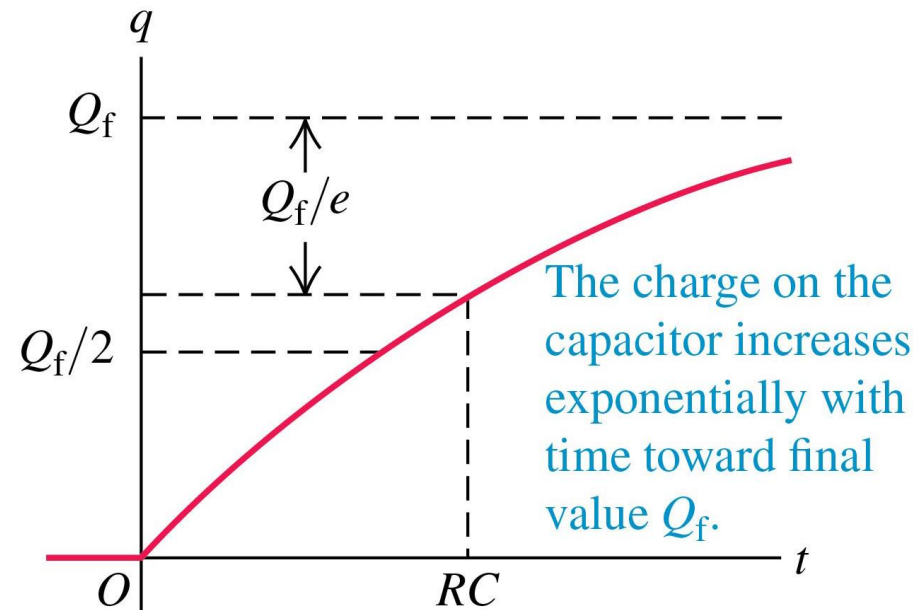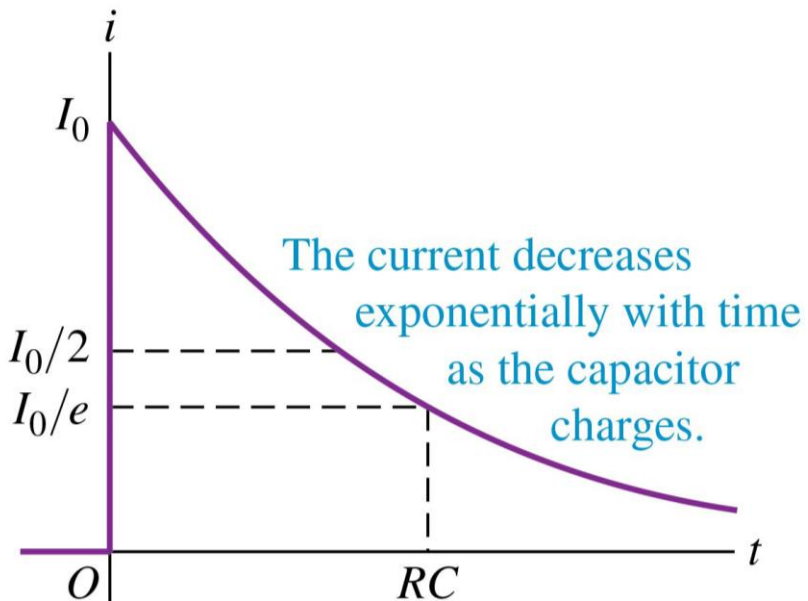
$$\boxed{i_c} = \frac{dq}{dt} = \frac{\varepsilon}{R} e^{-t/RC} = \boxed{I_0 e^{-t/RC}}$$



R-C circuits – Time constant τ


- When the time is equal to $t = \tau = RC$ then we have:

$$e^{-t/RC} = e^{-RC/RC} = e^{-1} = 0.368 = 36.8\%$$
- Therefore after time τ the current has been reduced to 36.8% of it's original value: $i_c = I_0 e^{-1} = \boxed{0.368 I_0}$
- In the same amount of time, the capacitor has charged to 63.2% of it's max charge: $q_c = Q_f(1 - e^{-1}) = \boxed{0.632 Q_f}$

Time	q_c	i_c
τ	63.2%	36.8%
2τ	86.5%	13.5%
3τ	95.0%	5.0%
4τ	98.2%	1.8%

R-C circuits – Discharging


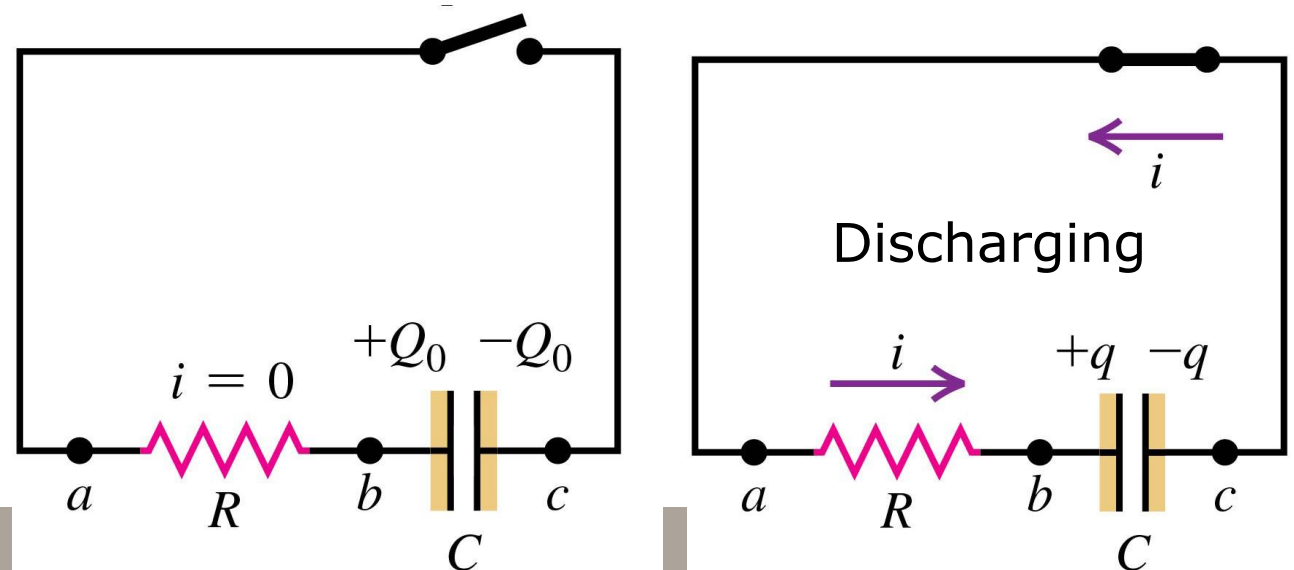
- The figures show a sample for **discharging a capacitor**.
- Before the switch is closed, the capacitor is at charge $q = Q_0$ and the current is $i = 0$.
- When the switch is closed, the capacitor discharges through the resistor. The initial current is $I_0 = -Q_0/RC$.
- Both the charge on the capacitor and the current in the circuit will slowly decrease until they reach 0.



R-C circuits – Discharging

- We perform same analysis as before but with equation $iR - \frac{q}{C} = 0$ then solve for i and set $i = dq/dt$. Separate dq and dt then integrate both sides.
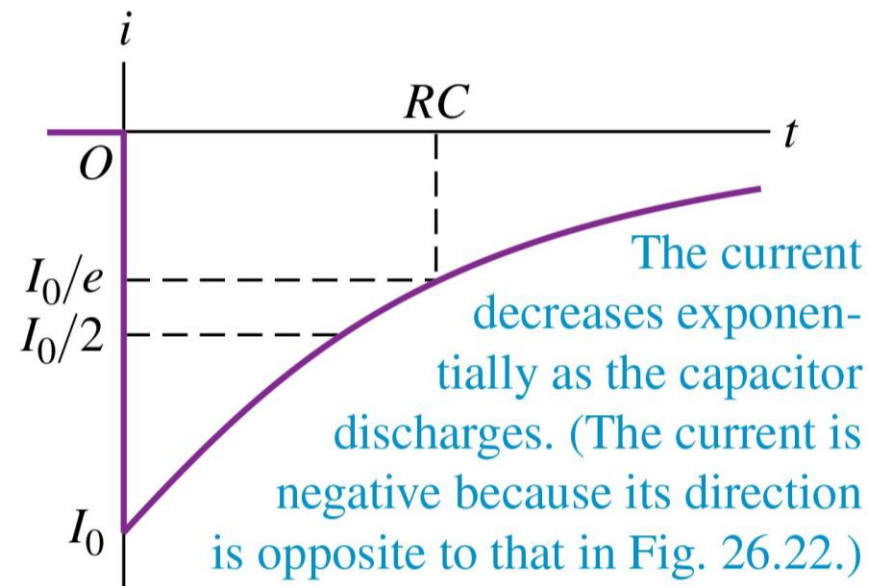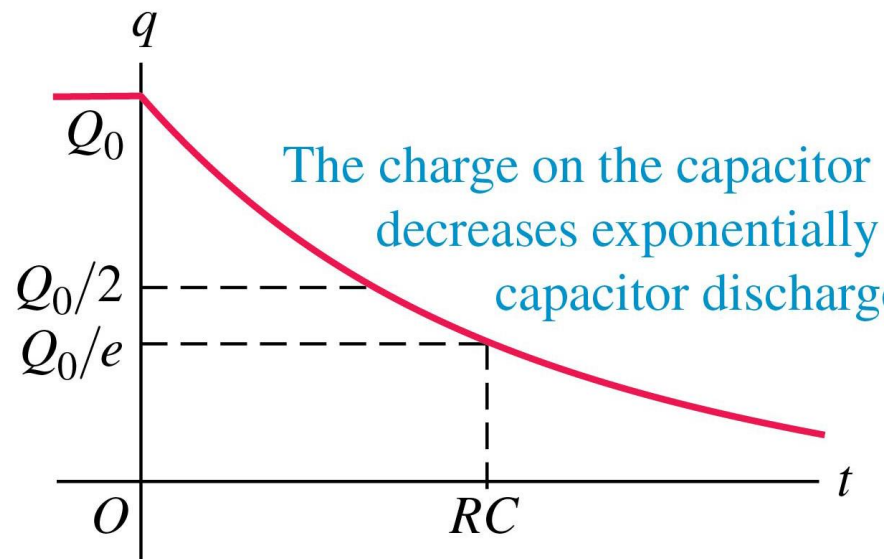
$$q_d = Q_0 e^{-t/RC} \quad \text{and} \quad i_d = I_0 e^{-t/RC}$$



R-C circuits – Energy and power

- Recall equations for power for emf/resistor/capacitor:

$$P = V_{ab}I = I^2R = \frac{Q}{C}I$$

- In this case, **power** is rate at which energy is delivered. For the RC circuit we get:

$$P = \varepsilon i = i^2R + \frac{iq}{C}$$

- **battery** delivers energy to circuit: $\boxed{\varepsilon i}$
- electrical energy is dissipated in **resistor**: $\boxed{i^2R}$
- energy is stored in the **capacitor**: $\boxed{iq/C}$