

## Chapter 25

- Current, Resistance, and Electromotive Force

Michael Wong – PHY 1122 Spring 2023

# Learning goals

- Meaning of **electric current** and how charges move in a conductor.
- Calculating **resistance**.
- How **electromotive force (emf)** makes current flow.
- **Energy** and **power** in electrical circuits.

# Electric circuits


- **Electric circuits** are used in every electronic device (TV, computer, calculator, etc...).
- In a closed circuit, charges can flow through conducting wires (typically electrons).
- **Resistors** are used to control the rate of charge flow.
  - 2<sup>nd</sup> circuit element we see (1<sup>st</sup> was capacitor).
- A **battery** can transfer charge and energy to a “load” (like a lightbulb).
  - The current flowing into the load is equal to current flowing out of it.

# Electric current

- An **electric current** is the flow of charge from one region to another (think of current in a stream). The charged particles that contribute to current are called **charge carriers**.
- The current (scalar) is defined to be the amount of charge  $dQ$  that passes through an area  $A$  in time  $dt$ :


$$I = \frac{dQ}{dt}$$

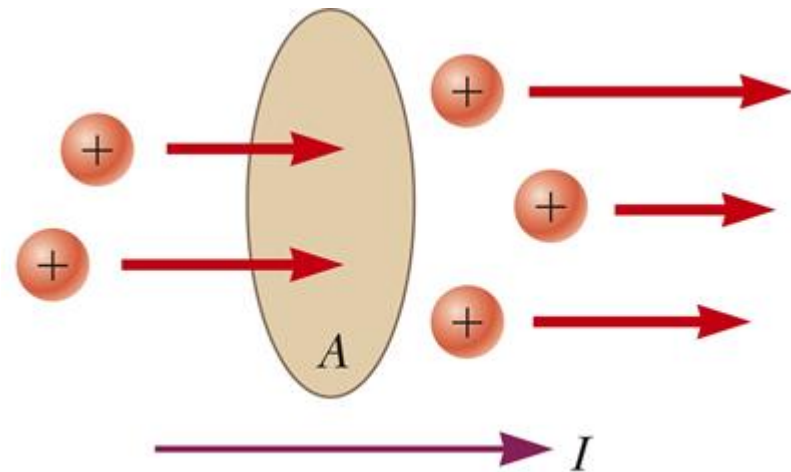- The SI unit of current is the ampere:  $1 \text{ A} = 1 \text{ C/s}$


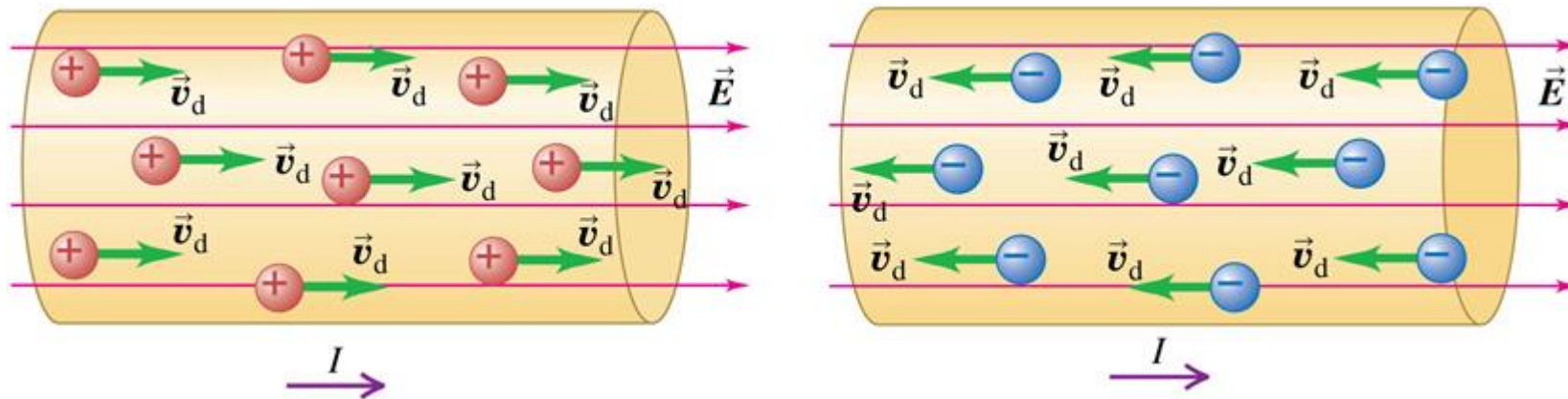
# Direction of current

- Current can be produced by the flow of positive, negative, or a combination of both charges.
- The convention we use: current is in direction of  $+q's$ .
- In a normal electric circuit, charge carriers (electrons) move opposite the direction of current.



# Drift speed of charge carriers


- In a thin slice of wire with area  $A$ , thickness  $v_d dt$ , there are  $n$  carriers per volume. The total charge in this area is:

$$dQ = q(nAv_d dt)$$

- Therefore the current, in terms of geometric components, is:

$$I = \frac{dQ}{dt} = nqAv_d$$

$$v_d = \frac{I}{nqA}$$


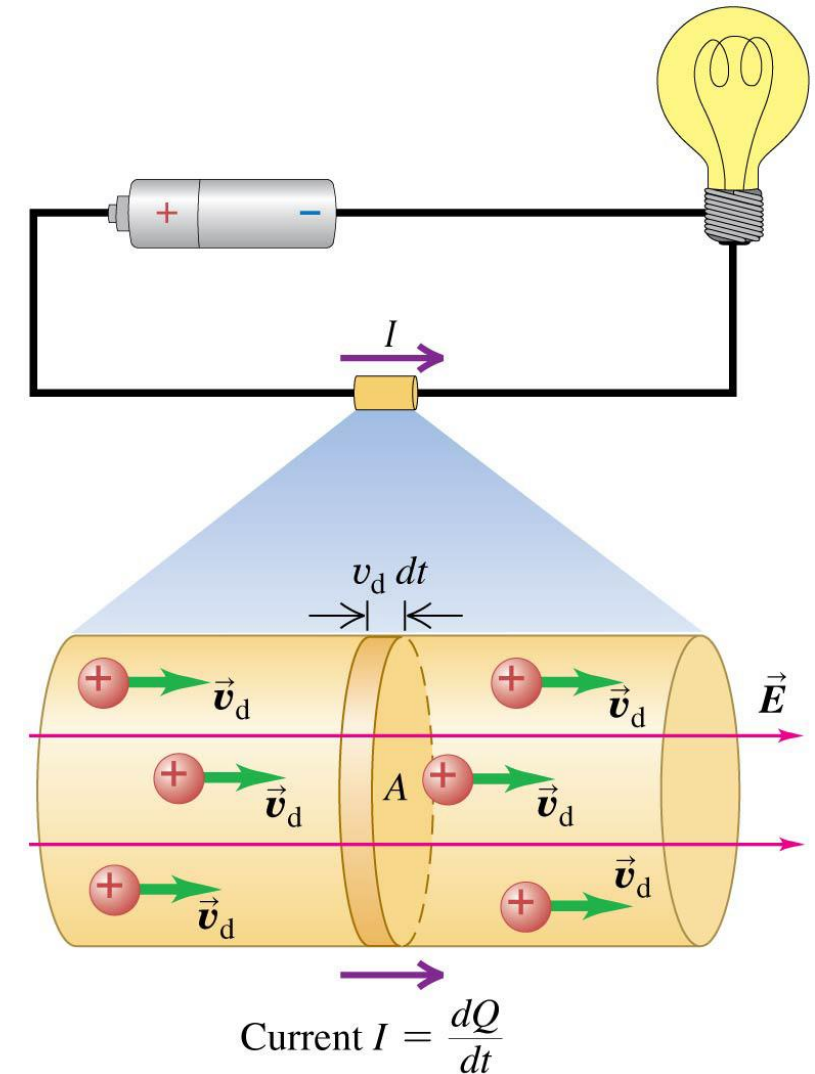


# Current density

- The **current density** (vector) is defined as the current per unit area and includes drift velocity:

$$\vec{J} = \frac{I}{A} = \frac{nqA\vec{v}_d}{A} = nq\vec{v}_d$$

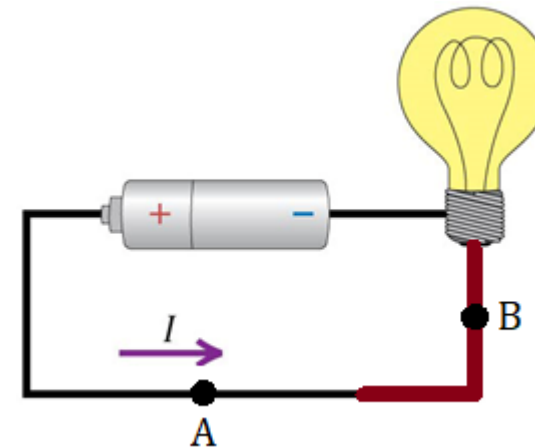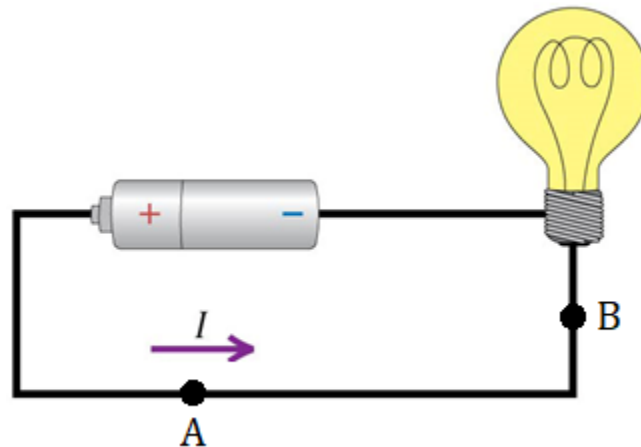- Current density is always in the same direction as the electric field.
  - It describes how charges flow at a given point.



## Ex. 25.1 - Current density and drift velocity in a wire


- An 18-gauge copper wire has diameter of 1.02 mm and carries a constant current of 1.67 A to a 200 W lamp. The free electron density in the wire is  $8.5 \times 10^{28} \text{ 1/m}^3$ .

- Find the magnitude of the current density.
- Find the drift speed.

$$A = \pi \left( \frac{d}{2} \right)^2 = 8.17 \times 10^{-7} \text{ m}^2$$

$$J = \frac{I}{A} = 2.04 \times 10^6 \frac{\text{A}}{\text{m}^2}$$
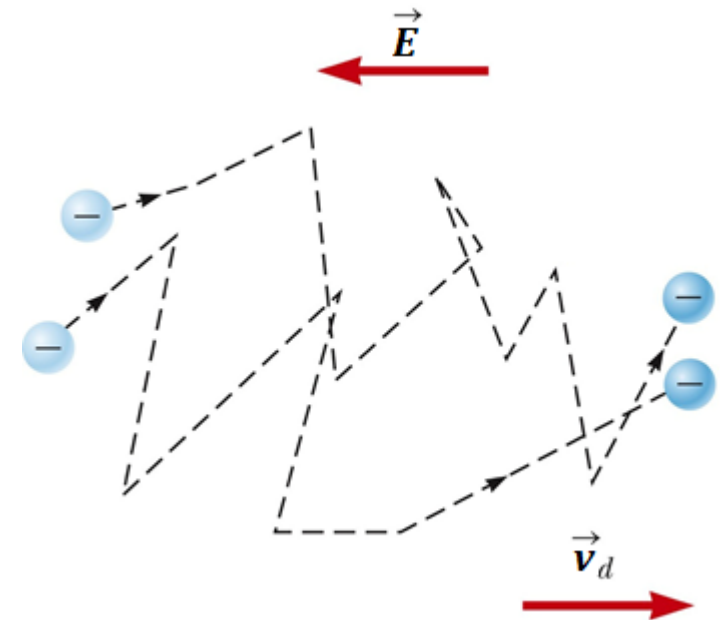
$$v_d = \frac{J}{nq} = 1.5 \times 10^{-4} \text{ m/s (about 0.15 mm/s)}$$





# Resistivity

- Current density in a conductor depends on electric field and on material properties.
- For some materials,  $\vec{J} \propto \vec{E}$ . These materials are said to be “ohmic” and follow **Ohm’s law**:

$$\boxed{J = \sigma E} \quad \text{or} \quad \boxed{E = \rho J}$$

where  $\sigma$  is the **conductivity** and  $\rho$  is the **resistivity**.


- A perfect conductor has  $\rho = 0$  and perfect insulator:  $\rho = \infty$ .
- The SI unit for resistivity is  $\Omega \cdot \text{m}$ .

## Some resistivities at $T = 20^\circ\text{C}$

	Substance	$\rho$ ( $\Omega \cdot \text{m}$ )
<b>Conductors</b>	Copper	$1.72 \times 10^{-8}$
	Gold	$2.44 \times 10^{-8}$
	Lead	$22 \times 10^{-8}$
<b>Semiconductor:</b>	Pure carbon (graphite)	$3.5 \times 10^{-5}$
<b>Insulators</b>	Glass	$10^{10} - 10^{14}$
	Teflon	$>10^{13}$
	Wood	$10^8 - 10^{11}$
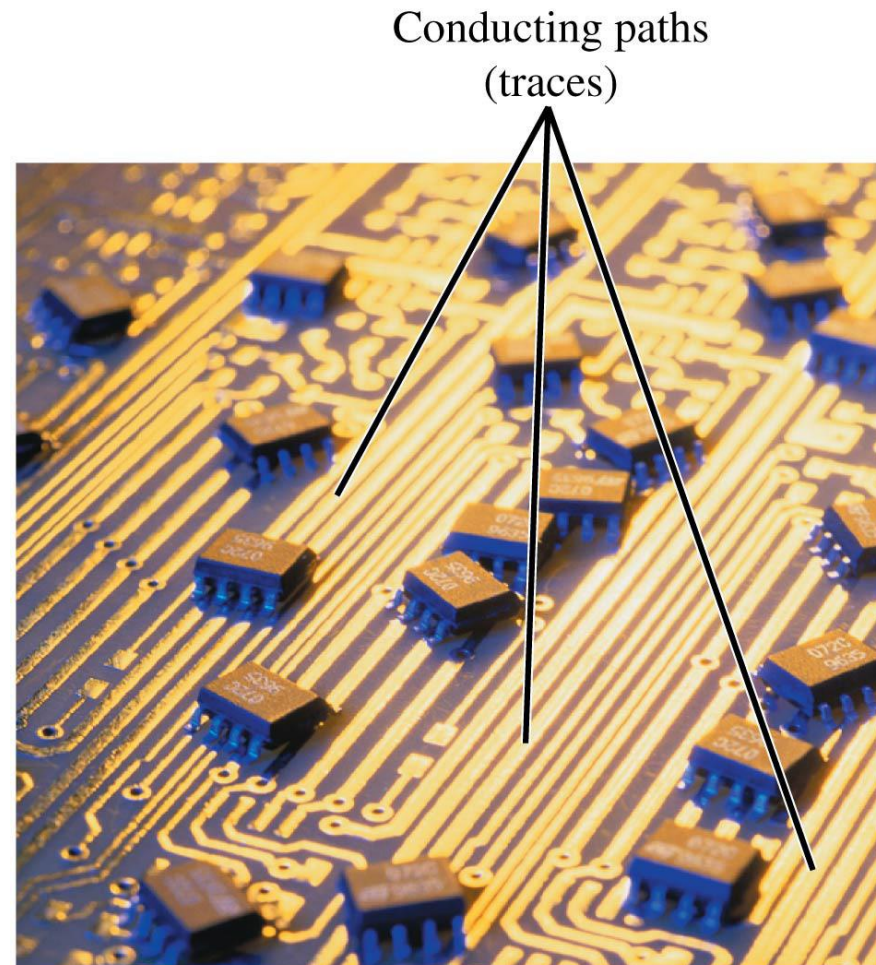
# Circuits boards and resistivity

- Copper “wires” or traces can be printed directly onto a circuit board’s surface.
- The traces can be extremely close together but the board has high resistivity so current can’t flow from trace to trace.




# Resistivity and temperature

- Resistivity of a metallic conductor (almost) always increases with temperature.
- At higher  $T$ , ions in a conductor vibrate more so chance of electron collision with an ion is higher.

- The temperature dependence equation for resistivity is:



$$\boxed{\rho(T) = \rho_0[1 + \alpha(T - T_0)]}$$

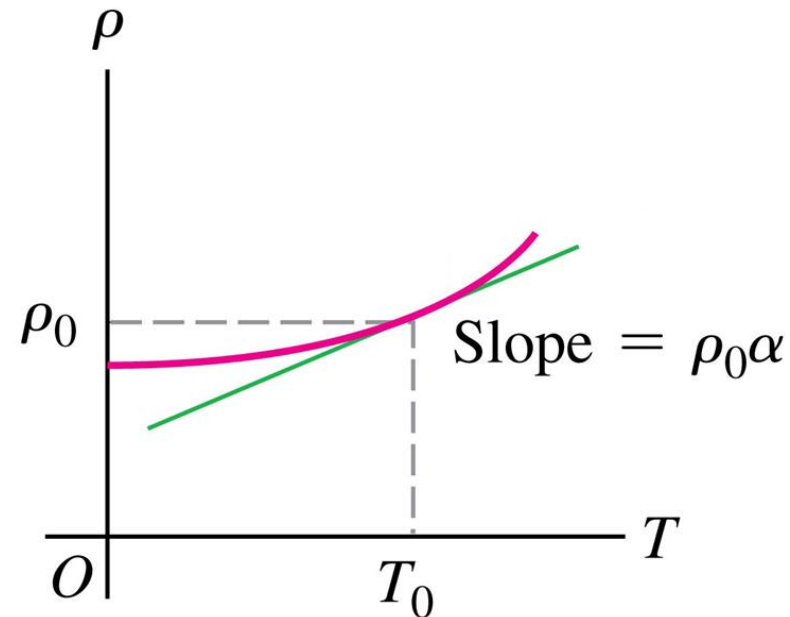where  $\alpha$  is the temperature coefficient.


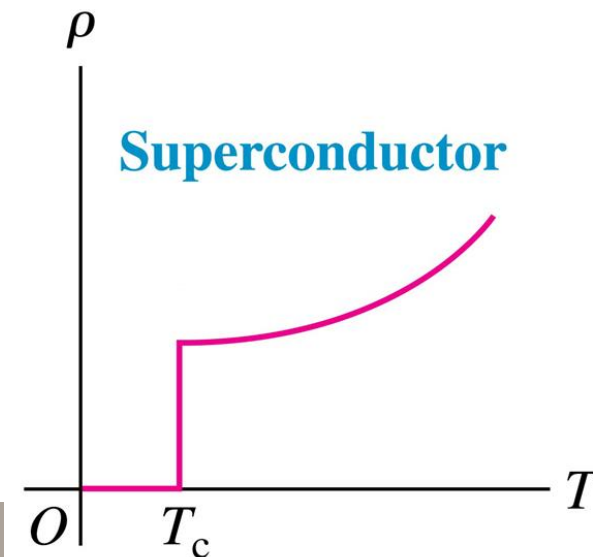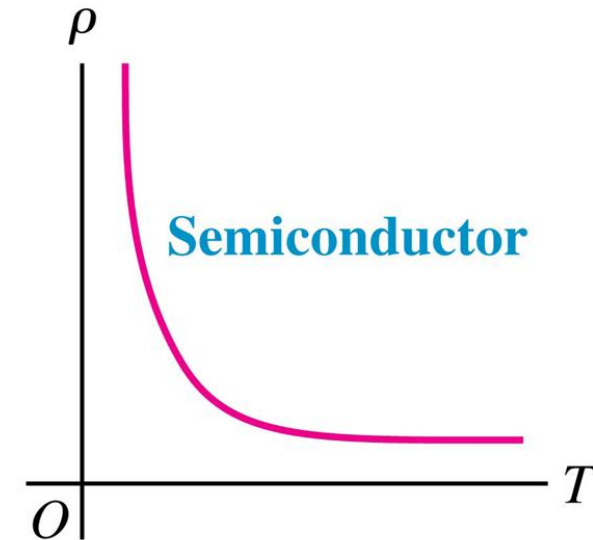
# Resistivity and temperature

- For some materials, resistivity decreases for higher  $T$  (such as graphite, a semiconductor where  $\alpha$  is negative).
  - Electrons “shake loose” when atoms are excited.
- Some materials display a phenomenon called “superconductivity” where below a critical temperature,  $T_c$ , the resistivity drops to virtually 0.
  - For Hg,  $T_c = 4.15$  K, and  $\rho_{sc} = 10^{-28} \Omega \cdot \text{m}$ .



# Ohm's law and resistance


- Recall: Ohm's law  $\vec{E} = \rho \vec{J}$ .
  - Electric field and current density are hard to measure.
  - We might be more interested in  $V$  and  $I$ .

- For a conductor with length  $L$ , resistivity  $\rho$ , and area  $A$ .

$$J = \frac{I}{A} \quad \text{and} \quad E = \frac{V}{L}$$

- Put these into equation above to get:

$$\boxed{V = \frac{\rho L}{A} I}$$

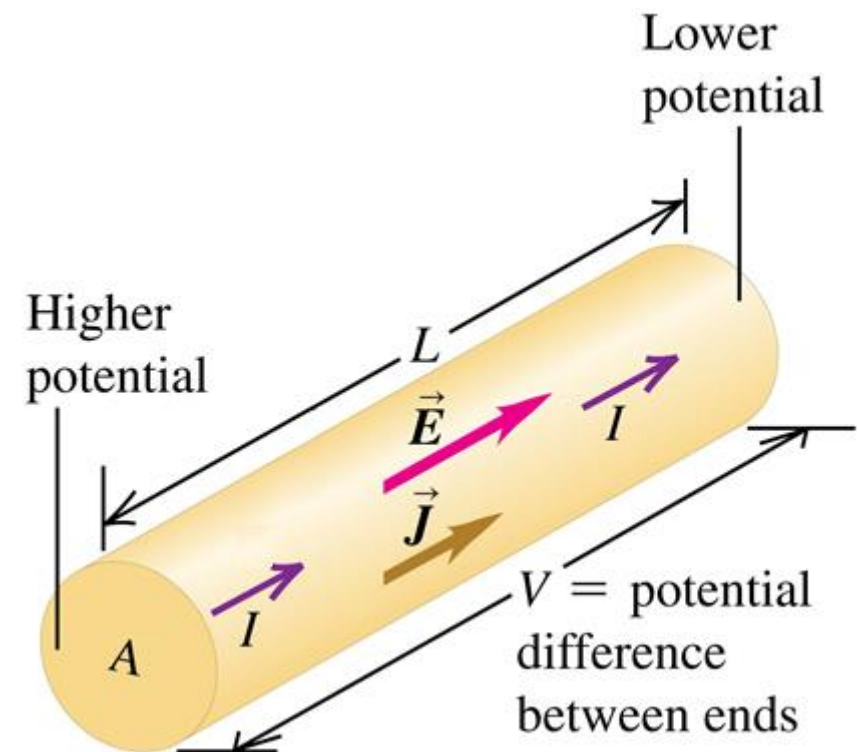

# Ohm's law and resistance

- Our Ohm's law relation has now been reduced to:

$$V = \frac{\rho L}{A} I$$


where the proportionality constant between  $V$  and  $I$  is called the **resistance**:

$$\boxed{R = \rho L / A} \text{ with unit Ohm } (\Omega).$$

- This gives us a **new form for Ohm's law** which you might have seen before:


$$\boxed{V = RI}$$

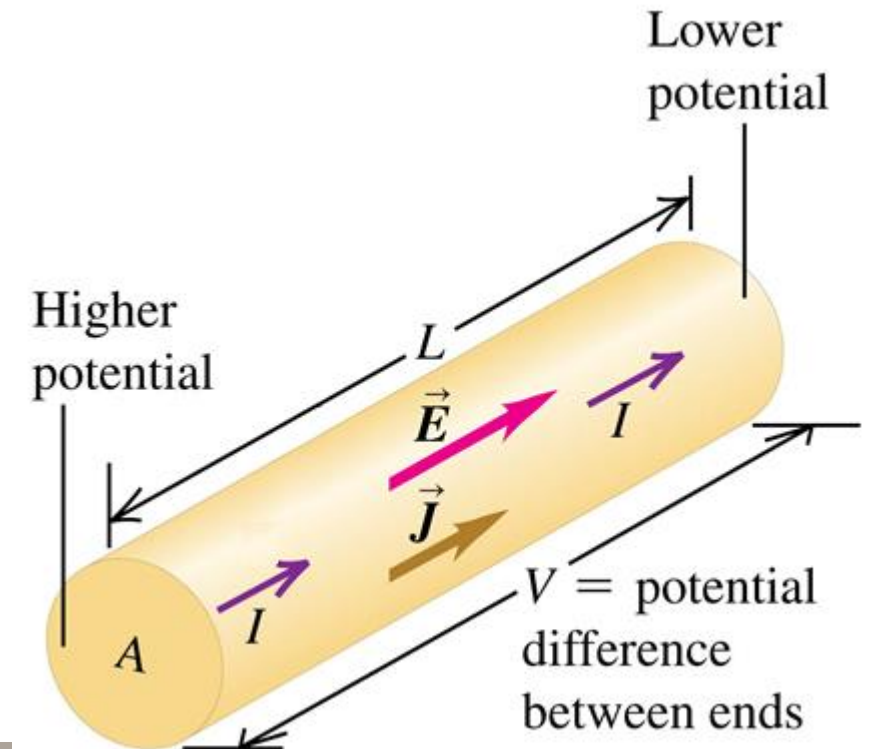which is much easier to verify in a lab setting.


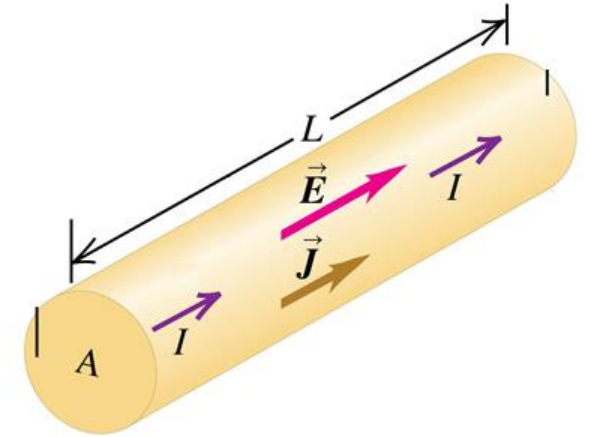
# Properties of resistance

- Resistance  $R = V/I$  and resistivity  $\rho$  are similar but different.
  - Resistance is for specific unit of a conductor
  - Resistivity is inherent to type of conductor (or metal).
- Resistance also increases with temperature for a large range:
 
$$R(T) = R_0[1 + \alpha(T - T_0)]$$
  - We can exploit this to make very sensitive temperature probes (**resistance thermometers**).
- The SI unit of resistance: 1 **ohm** ( $\Omega$ ) = 1 V/A .
- A **resistor** is a circuit device that has a specific resistance  $R$ .





## Ex. 25.2 – Field, potential, and $R$

- The 18-gauge copper wire with diameter 1.02 mm carries current of 1.67 A.
  - (a) Find the magnitude of the electric field in the wire.
  - (b) find the potential difference between two points that are 50.0 m apart in the wire.
  - (c) Find the resistance of a 50.0 m length of this wire.

**NB:**  $\rho_{\text{Cu}} = 1.72 \times 10^{-8} \Omega \cdot \text{m}$


# Electromotive force and circuits

- Just like a water fountain needs a pump, an electric circuit needs a source of **electromotive force (emf)** to sustain current.



# Electromotive force and circuits

- In order to have a steady current, a circuit must be a **closed loop**.
- If you apply a field  $\vec{E}_1$  to an isolated conductor, the field moves charges which creates a second field  $\vec{E}_2$  in opposite direction.
  - Eventually you will have  $|\vec{E}_1| = |\vec{E}_2|$  and the flow of charges stops.
  - No collective flow of charge means no current.

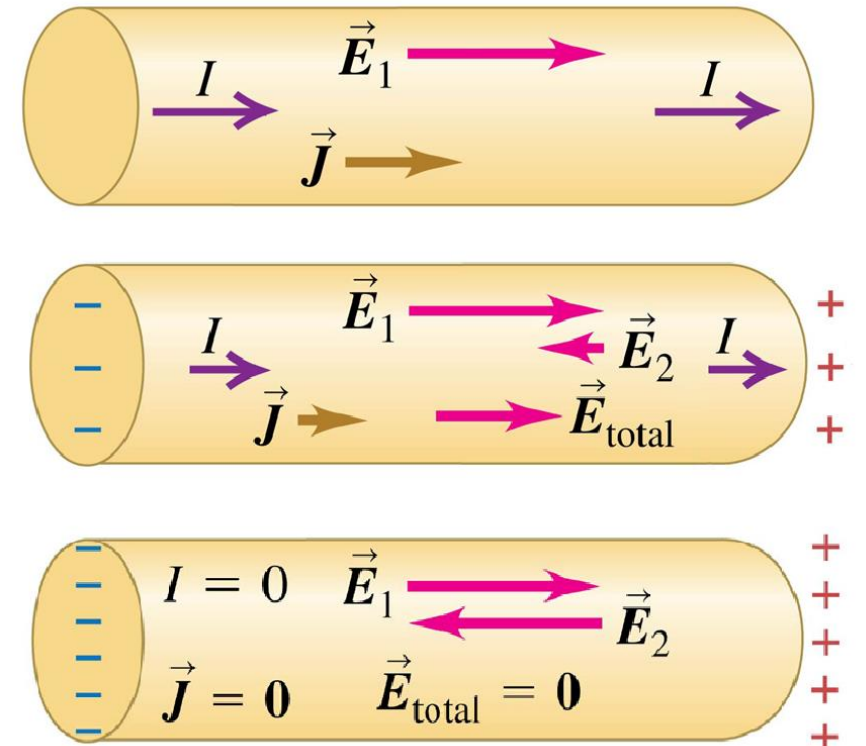

## Electromotive force and circuits


- A **battery** or **power supply** is a source of electromotive force (**emf**,  $\varepsilon$ ) and supplies a potential difference in the circuit to allow charge to flow.
  - **NB.** Emf is not a force, it's energy per charge (unit V).
- A typical flashlight uses two AA batteries in series. Each battery provides 1.5 V of emf.
  - I.e. Each battery does 1.5 J of work on each C of charge.
  - Also means the potential difference between the ends of the AA battery is 1.5 V.

# Internal resistance in a circuit

- Real sources of emf contain **internal resistance**  $r$ .
- A 12 V power supply has terminal voltage  $V_{ab}$  when it is connected to the lightbulb:

$$V_{ab} = \varepsilon - Ir$$

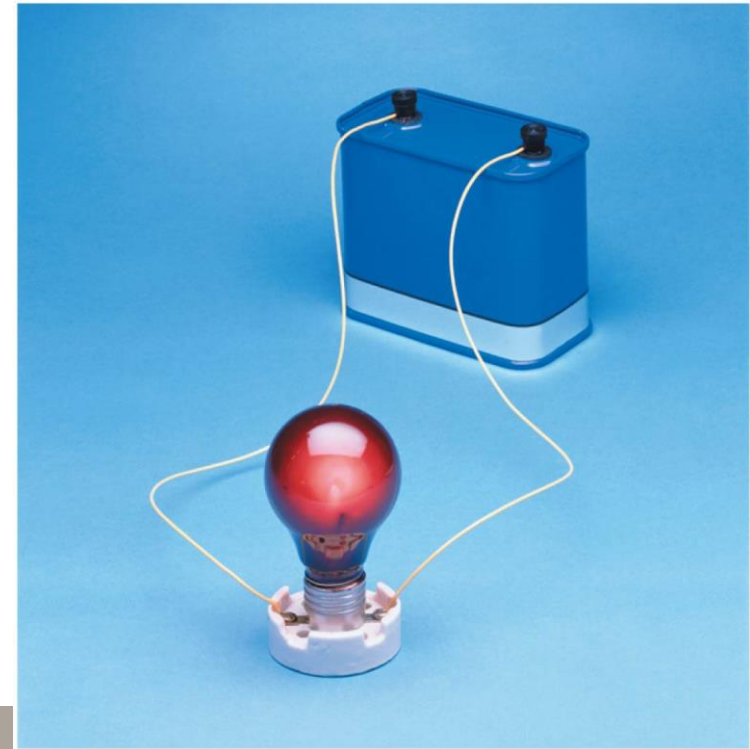
- Typically,  $r \ll R$  in most electronic devices
  - Example in the image:  
 $R$  of the lightbulb is  $\sim 250 \Omega$ .  
 $r$  of the power supply is  $\sim 2 \Omega$ .


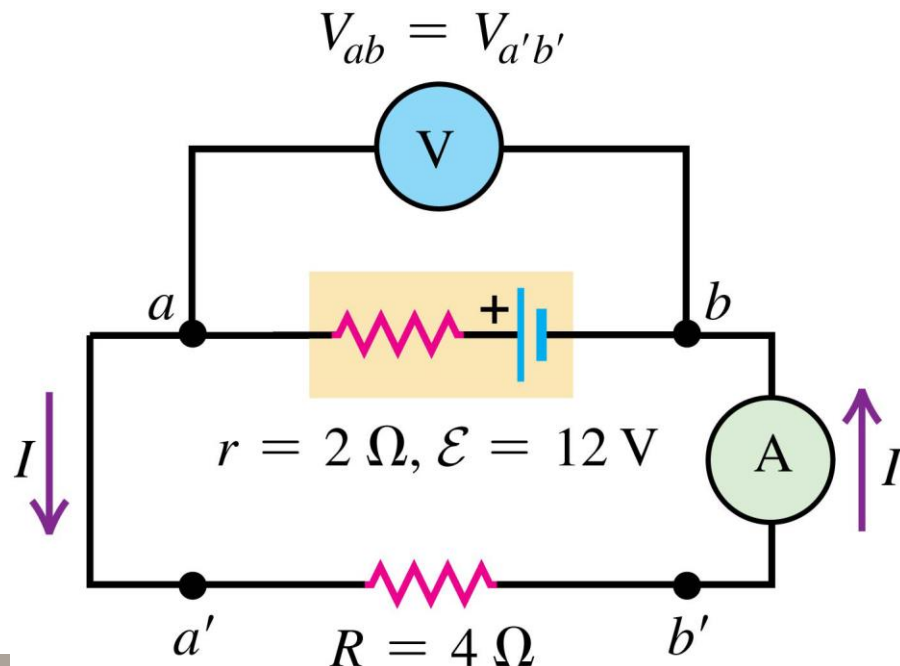
## Ex. 25.5 – A source in a complete circuit

- A battery with emf  $\varepsilon = 12\text{ V}$  and internal resistance  $r = 2\ \Omega$  is connected to a resistor  $R = 4\ \Omega$  as shown.

Determine the readings of the voltmeter (measuring  $V_{ab}$ ) and the ammeter (measuring  $I$ ).



Solution:

$$V_{ab} = \varepsilon - Ir = V_{a'b'} = IR$$


$$\boxed{I} = \frac{\varepsilon}{r + R} = \frac{12\text{ V}}{6\ \Omega} = \boxed{2.0\text{ A}}$$

$$\boxed{V_{ab}} = 12\text{ V} - (2.0\text{ A})(2\ \Omega) = \boxed{8.0\text{ V}}$$
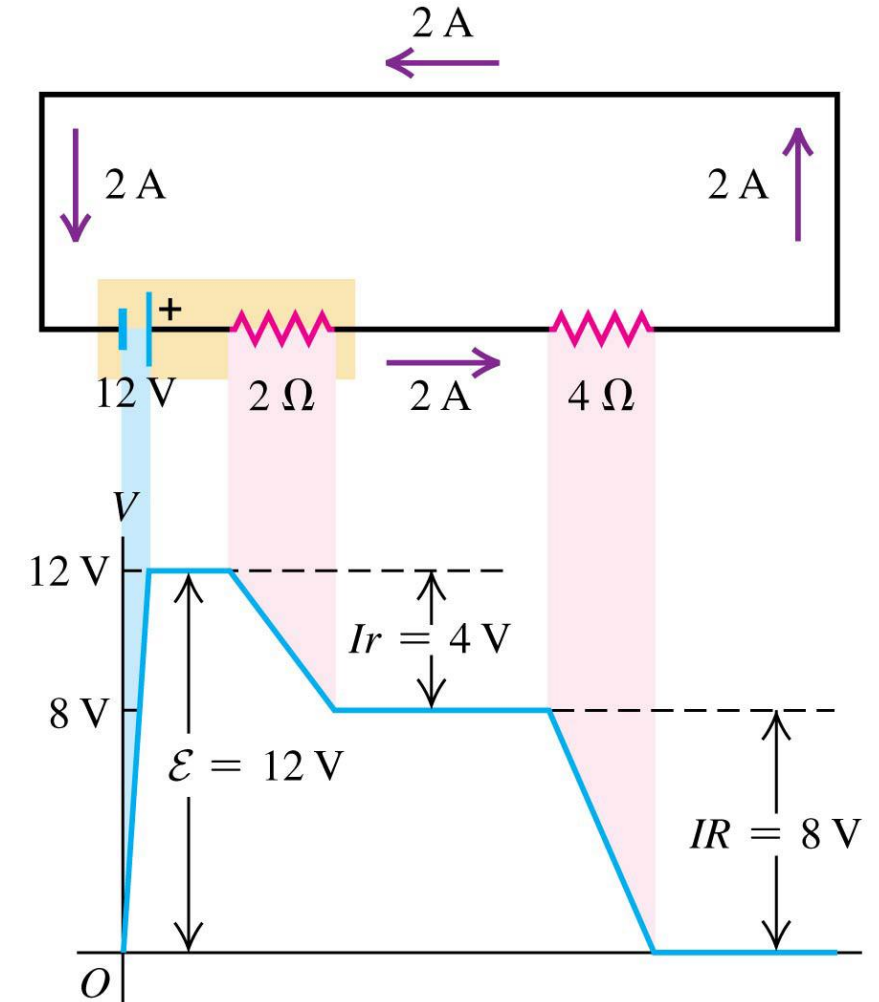
# Potential changes around a circuit


- For the circuit shown:  $I = V/R = 12/6 = 2 \text{ A}$
- In a closed circuit, the net change in potential must be equal to zero:  

$$\boxed{\Sigma \Delta V} = \varepsilon - Ir - IR = \boxed{0}$$
- Note: the current is the same at all parts in this "circuit" because all elements are in series.
- We will see this net zero potential again in Ch. 26 when we study **Kirchhoff's rules**.


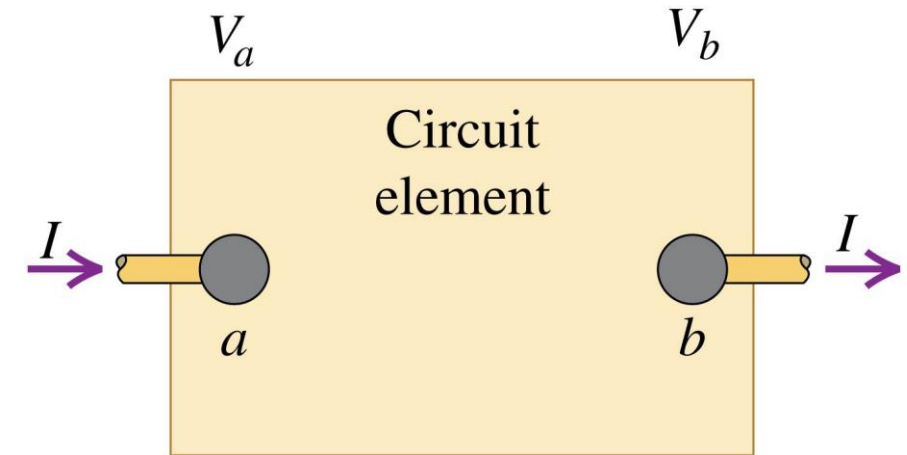
# Energy and power in circuits

- The box represents a circuit element with  $V_{ab} = V_a - V_b$  and current  $I$  passing through it.
- If  $V_b < V_a$ , we have energy transfer **in** to the element (like a toaster).
  - If  $V_a < V_b$ , energy is transferred *out* of the element (like a battery).
- Power** is the rate of change of energy transfer:
 
$$P = V_{ab}I$$
  - Measured in **watts**:  $1 \text{ W} = 1 \text{ J/s}$



The units:

$$\boxed{\text{W}} = \text{V} \cdot \text{A} = \frac{\text{J}}{\text{C}} \cdot \frac{\text{C}}{\text{s}} = \boxed{\frac{\text{J}}{\text{s}}}$$




## Power and energy to a resistor

- The power ( $P = V_{ab}I$ ) to a resistor ( $V_{ab} = IR$ ) is given by:

$$P = I^2R = \frac{V^2}{R}$$

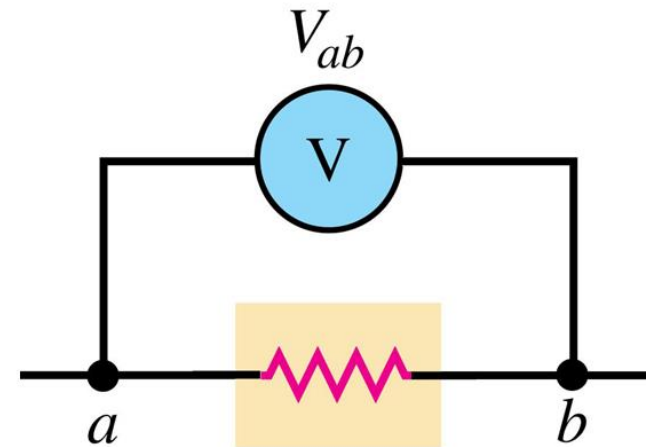- The potential is always higher before the resistor (point  $a$ ) than after (point  $b$ ) for current moving from  $a$  to  $b$ .
- The energy transferred into a resistor makes it hot. Some resistor systems (eg. space heaters, toasters) are designed to get hot and due to resistive heating and transfer heat into its surroundings.



# Power to/from an emf source

- Power can be output *from* a source (like a battery powering a flashlight):



$$\boxed{P} = V_{ab}I = \boxed{(\varepsilon - Ir)I}$$

Work is being done by the source to move the charges through the light.

- Power can also be input *to* a source (alternator charging a car battery):

$$\boxed{P} = V_{ba}I = \boxed{(\varepsilon + Ir)I}$$

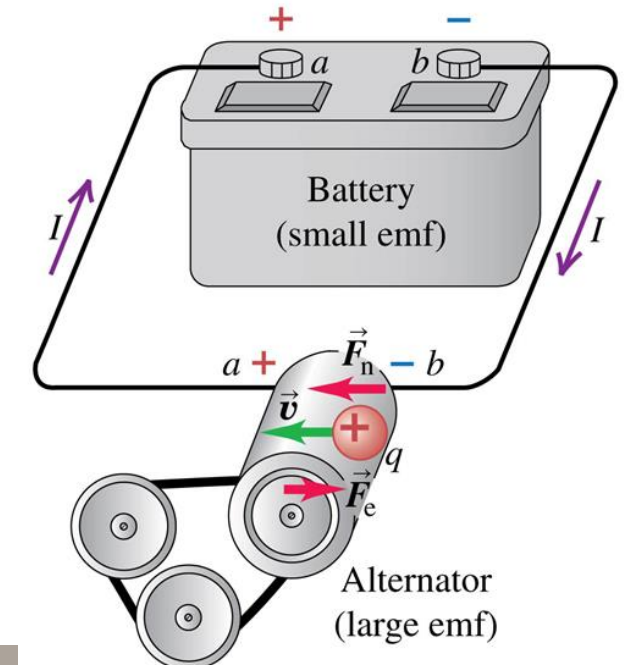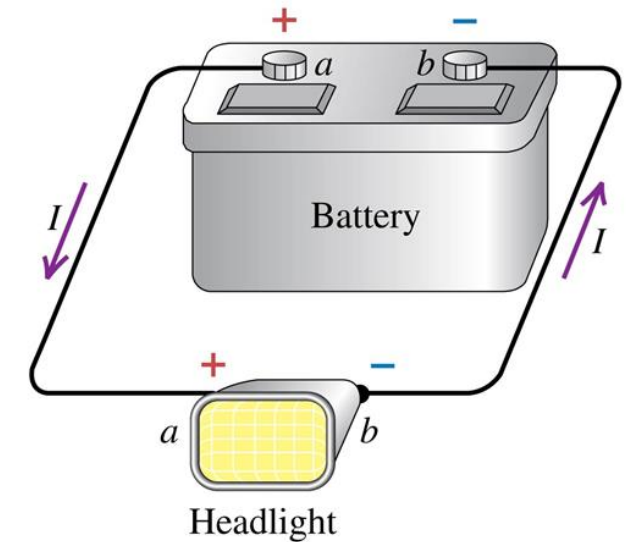Source with larger emf works on and delivered energy to smaller emf.



## Exs. 25.8-10 – Power in a circuit

- **25.8:** Find the rate of **energy conversion (energy transfer)** and **energy dissipation** in the circuit below (left figure) for each element as well as the net power output of the battery.
- **25.9:** What if the  $4\ \Omega$  resistor was replaced with an  $8\ \Omega$  one?
- **25.10:** What if the resistor was removed (right figure)?

